

## FLIP-FLOP

Aim:- Truth table verification of Flip-Flops:

### RS FLIP-FLOP

- (i) JK Master Slave
- (ii) D- Type
- (iii) T- Type.

Apparatus Required: -

IC 7410, IC 7400, etc.

Procedure: -

1. Connections are made as per circuit diagram.
2. The truth table is verified for various combinations of inputs.

Truth Table:- (Master Slave JK Flip-Flop)

Preset	Clear	J	K	Clock	$Q_{n+1}$	$\overline{Q_{n+1}}$	
0	1	X	X	X	1	0	Set
1	0	X	X	X	0	1	Reset
1	1	0	0	$\downarrow$	$Q_n$	$\overline{Q_n}$	No Change
1	1	0	1	$\downarrow$	0	1	Reset
1	1	1	0	$\downarrow$	1	0	Set
1	1	1	1	$\downarrow$	$\overline{Q_n}$	$Q_n$	Toggle

D Flip-Flop:-



Preset	Clear	D	Clock	$Q_{n+1}$	$\overline{Q_{n+1}}$
1	1	0	$\square$	0	1
1	1	1	$\square$	1	0


T Flip-Flop:-

Preset	Clear	T	Clock	$Q_{n+1}$	$\overline{Q_{n+1}}$
1	1	0	$\square$	$Q_n$	$\overline{Q_n}$
1	1	1	$\square$	$\overline{Q_n}$	$Q_n$

Exercise:-

- Write the timing diagrams for all the above Flip-Flops


Pin Details:-

 

Truth Table:-

Clock	QC	QB	QA
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1


Timing Diagram:-

 



Preset	Clear	J	K	Clock	$Q_{n+1}$	$\overline{Q_{n+1}}$	
0	1	X	X	X	1	0	Set
1	0	X	X	X	0	1	Reset
1	1	0	0	$\neg$	$Q_n$	$\overline{Q_n}$	No Change
1	1	0	1	$\neg$	0	1	Reset
1	1	1	0	$\neg$	1	0	Set
1	1	1	1	$\neg$	$\overline{Q_n}$	$Q_n$	Toggle

(a) Connect the two NOR gates as shown in Figure 1.

 

**Figure 1.** An RS Flip-Flop created using NOR gates.


(b) Vary the inputs R and S (i.e. 0 and +5V) to obtain all the possible combinations for Q and /Q.

(c) In your opinion why is there a Q and /Q output? In your opinion how does this circuit work?


## Section 2. The Synchronous Flip-Flop

(a) Synchronous means that this flip-flop is concerned with time! Digital circuits can have a concept of time using a clock signal. The clock signal simply goes from low-to-high and high-to-low in a short period of time.



 

**Figure 2.** A typical clock signal.

 


**Figure 3.** The Synchronous Flip Flop.

Implement the circuit in Figure 3. You can simulate a clock signal by moving the clock line from low to high and back again to low.

(b) Vary inputs R and S and apply the clock pulse. Write the output states into a table as below:

$Q_n / Q_{n+1}$	R	S	$Q_{n+1} / Q_{n+1}$
0 1	0 0		
1 0	0 0		
0 1	0 1		
1 0	0 1		
0 1	1 0		
1 0	1 0		
0 1	1 1		
1 0	1 1		

(c) Convert the circuit into a D-type flip flop (as shown in Figure 4.)

 

**Figure 4.** The D-type flip-flop

Draw up the truth table for a D-type flip flop. In your opinion how does it work? what could this circuit be useful for?